

# Digital Logic Design

EE(1005)

Lecture- 30







# Chapter No:7

## Latches and Flip Flop



# FLIP-FLOP APPLICATIONS

## Parallel Data Storage

 
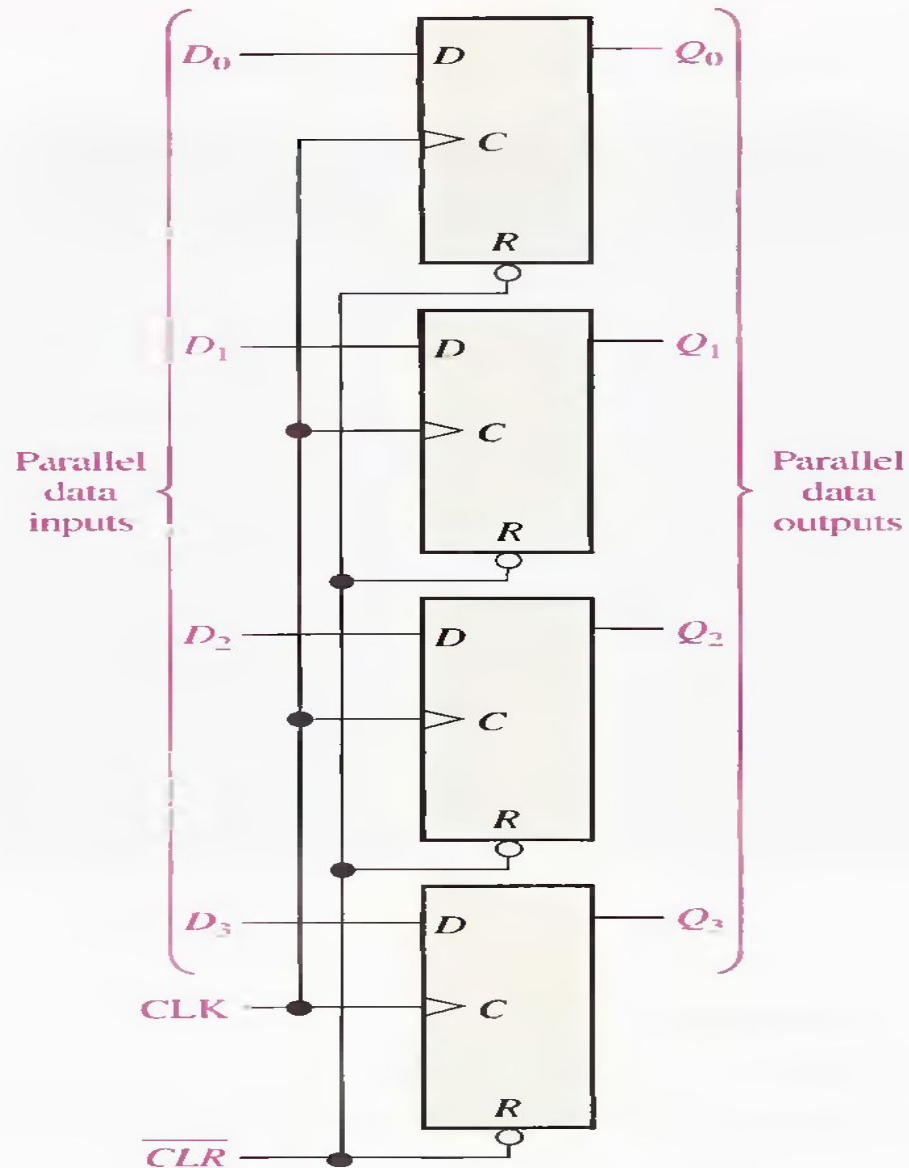

  
# Frequency Division


The J-K flip-flop as a divide-by-2 device.  $Q$  is one-half the frequency of CLK.



  
Example of two J-K flip-flops used to divide the clock frequency by 4.  $Q_A$  is one-half and  $Q_B$  is one-fourth the frequency of CLK.



 Develop the  $f_{out}$  waveform for the circuit in Figure when an 8 kHz square wave input is applied to the clock input of flip-flop A.



 The three flip-flops are connected to divide the input frequency by eight ( $2^3 = 8$ )



# Counting

Flip-flops used to generate a binary count sequence. Two repetitions (00, 01, 10, 11) are shown.

