Question:1 2 bit by 2 bit multiplier
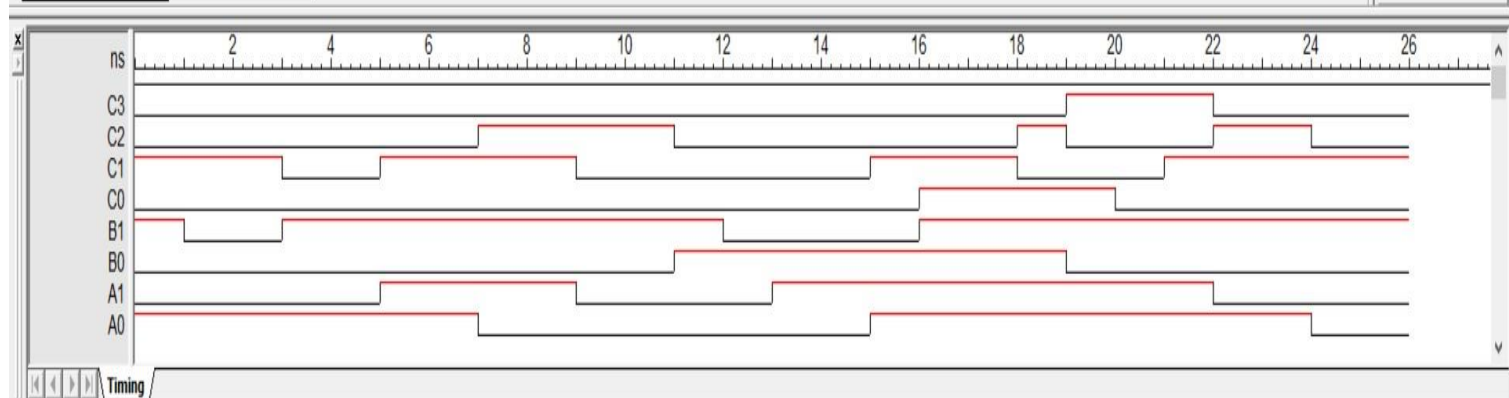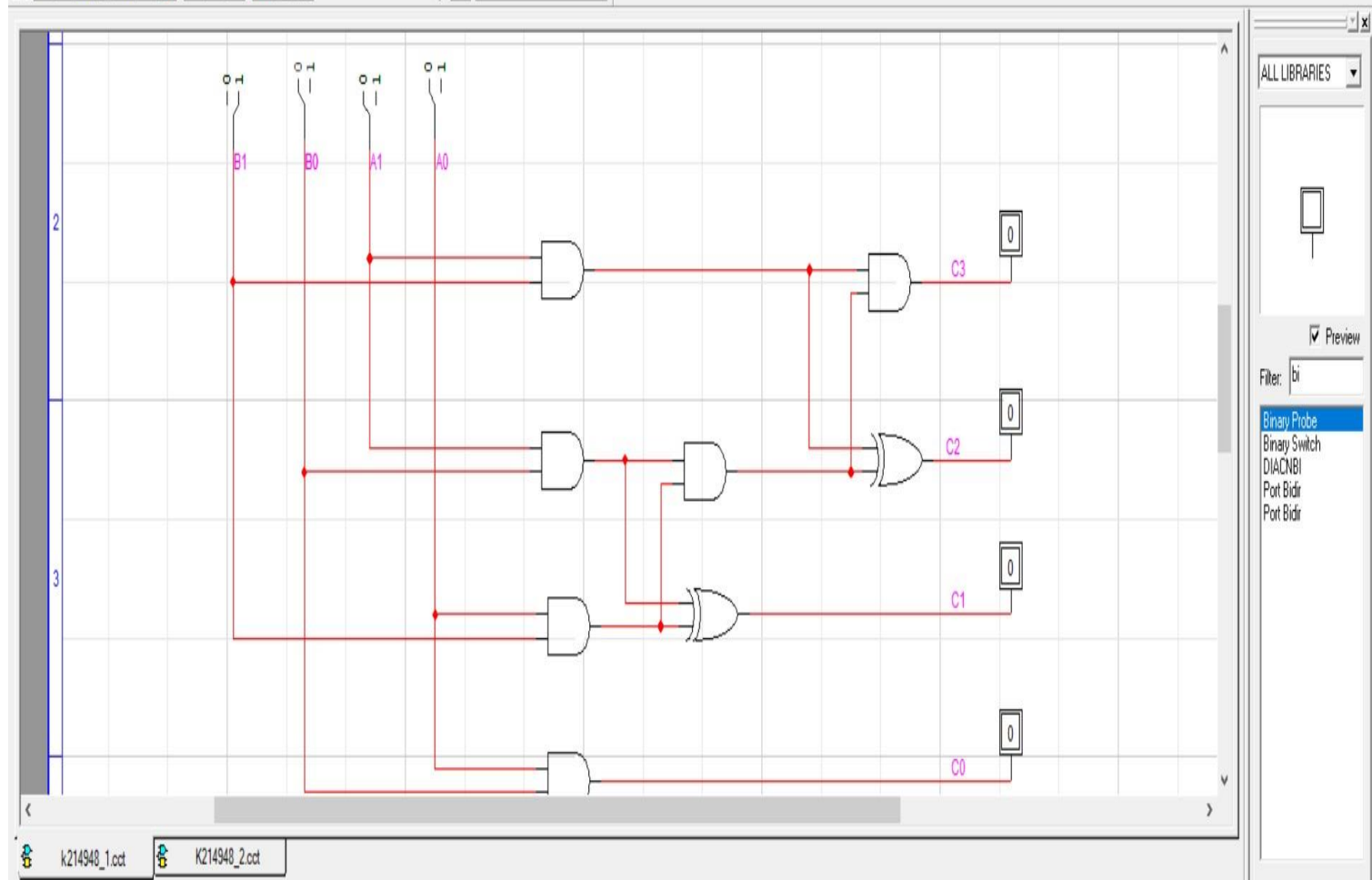
Question:2 3 bit by 3 bit multiplier